

Control systems(EE2101)

EE19BTECH11016
S.Naga Chandra Mouli

September 8th, 2020

Find the transfer function, $G(s) = V_o(s)/V_i(s)$ for each of the networks shown below, solve the problem using mesh analysis ?

1st circuit

Mesh analysis

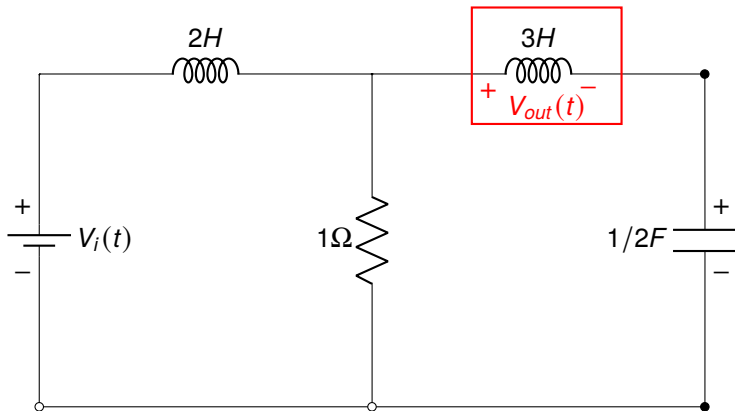


Figure: 1st circuit

by converting above circuit into frequency domain we get as below

consider the currents $I_1(s)$ and $I_2(s)$ in loop1 and loop2 respectively in clockwise direction

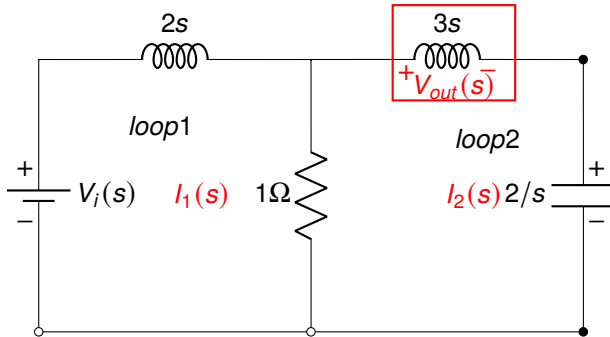


Figure: 1st circuit

solving mesh equations

loop1 and loop 2

- from loop1 we get

$$V_i(s) = 2sI_1(s) + 1(I_1(s) - I_2(s)) \quad (1)$$

$$V_i(s) = (2s + 1)I_1(s) - I_2(s) \quad (2)$$

- from loop2 we get

$$I_2(s)(3s + 2/s + 1) - I_1(s) = 0$$

$$I_2(s)(3s + 2/s + 1) = I_1(s)$$

$$V_0(s) = 3sI_2(s)$$

solving equations

substitution is enough

by substituting $I_2(s)$ in terms of $I_1(s)$ in equation(1) gives
and substitute $I_2(s)$ in terms of $V_{out}(s)$ we get

$$V_i(s) = (2s + 1)(3s + 2/s + 1)I_2(s) - I_2(s)$$

$$V_i(s) = [(2s + 1)(3s + 2/s + 1) - 1]I_2(s)$$

$$V_i(s) = [(2s + 1)(3s + 2/s + 1) - 1] \frac{V_{out}(s)}{3s}$$

$$\frac{V_{out}(s)}{V_i(s)} = \frac{3s^2}{6s^3 + 5s^2 + 4s + 2}$$

$$\boxed{G(s) = \frac{V_{out}(s)}{V_i(s)} = \frac{3s^2}{6s^3 + 5s^2 + 4s + 2}}$$

(3)

2nd circuit

Mesh analysis

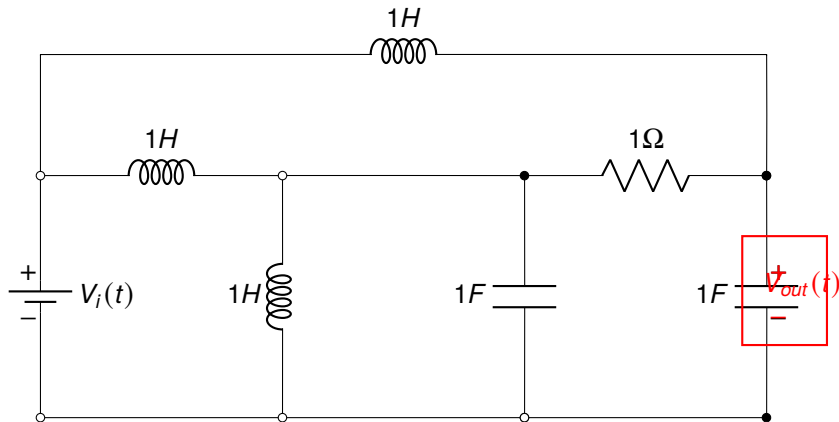


Figure: 2nd circuit

frequency domain

circuit simplification

by simplifying parallel combination of s and $1/s$ we get

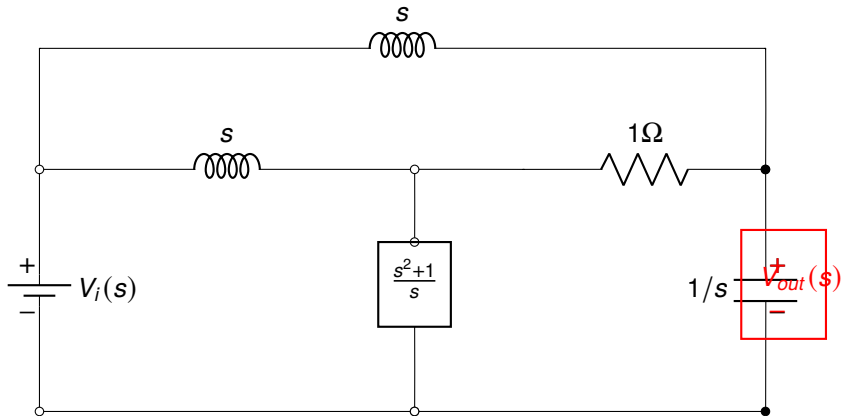


Figure: 2nd circuit

by converting above circuit into frequency domain we get as below

consider the currents $I_1(s)$ and $I_2(s)$ and $I_3(s)$ in loop1 and loop2 and loop3 respectively in clockwise direction

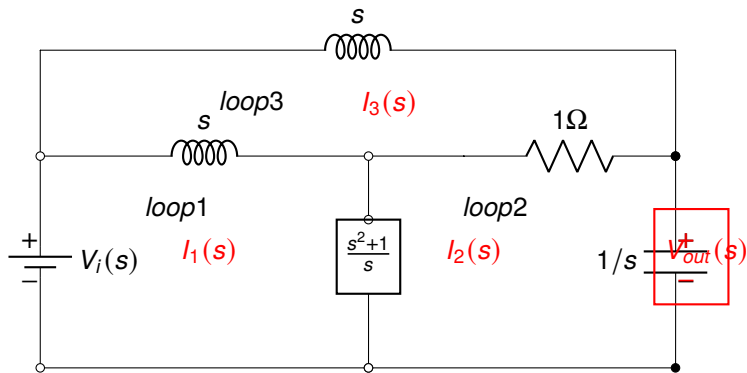


Figure: 2nd circuit

solving mesh equations

loop1 and loop 2 and loop3

- by solving loop equations we get

$$(s + \frac{s}{s^2 + 1})I_1(s) - (\frac{s}{s^2 + 1})I_2(s) - sI_3(s) = V_i(s)$$

$$-(\frac{s}{s^2 + 1})I_1(s) + (\frac{s}{s^2 + 1} + 1 + \frac{1}{s})I_2(s) - I_3(s) = 0$$

$$-sI_1(s) - I_2(s) + (2s + 1)I_3(s) = 0$$

$$V_{out}(s) = \frac{I_2(s)}{s}$$

$$\begin{bmatrix} s + \frac{s}{s^2 + 1} & -\frac{s}{s^2 + 1} & -s \\ -\frac{s}{s^2 + 1} & \frac{s}{s^2 + 1} + 1 + \frac{1}{s} & -1 \\ -s & -1 & 2s + 1 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_i(s) \\ 0 \\ 0 \end{bmatrix}$$

From Cramer's Rule,

$$I_1(s) = \frac{\Delta_1}{\Delta}, I_2(s) = \frac{\Delta_2}{\Delta}$$

$$I_3(s) = \frac{\Delta_3}{\Delta}$$

Cramers Rule

$$\Delta_2 = \begin{vmatrix} s + \frac{s}{s^2 + 1} & V_i(s) & -s \\ -\frac{s}{s^2 + 1} & 0 & -1 \\ -s & 0 & 2s + 1 \end{vmatrix}$$

$$= V_i(s) \left[s \left(\frac{2s + 1}{s^2 + 1} + 1 \right) \right]$$

$$\Delta_2 = s V_i(s) \frac{s^2 + 2s + 2}{s^2 + 1}$$

$$\Delta = \begin{vmatrix} s + \frac{s}{s^2 + 1} & -\frac{s}{s^2 + 1} & -s \\ -\frac{s}{s^2 + 1} & \frac{s}{s^2 + 1} + 1 + \frac{1}{s} & -1 \\ -s & -1 & 2s + 1 \end{vmatrix}$$

$$\Delta = \frac{s^4 + 2s^3 + 3s^2 + 3s + 2}{s^2 + 1}$$

$$I_2(s) = \frac{\Delta_2}{\Delta}$$

$$V_{out}(s) = \frac{I_2(s)}{s}$$

$$I_2(s) = \frac{V_i(s)s(s^2 + 2s + 2)}{s^4 + 2s^3 + 3s^2 + 3s + 2}$$

$$V_{out}(s) = \frac{V_i(s)(s^2 + 2s + 2)}{s^4 + 2s^3 + 3s^2 + 3s + 2}$$

$$\frac{V_{out}(s)}{V_i(s)} = \frac{(s^2 + 2s + 2)}{s^4 + 2s^3 + 3s^2 + 3s + 2}$$

$$G(s) = \frac{(s^2 + 2s + 2)}{s^4 + 2s^3 + 3s^2 + 3s + 2}$$

The End